## **Assignment 2**


Due on Mon Oct 26th at 10:00 pm


Name: Elaf Yousef Aloufi	
ID: 1911265	
Section: VAR	

Design a counter Using T ff's. This counter should count down from 7 to 0 to 7. The circuit counts downward with sequence **111,110,101,100,011,010,001,000** and then the count repeats.
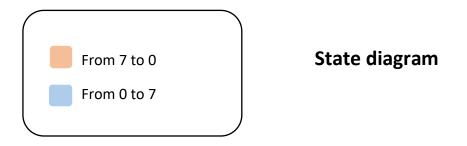
## You will need to:

- Derive the state diagram and state table



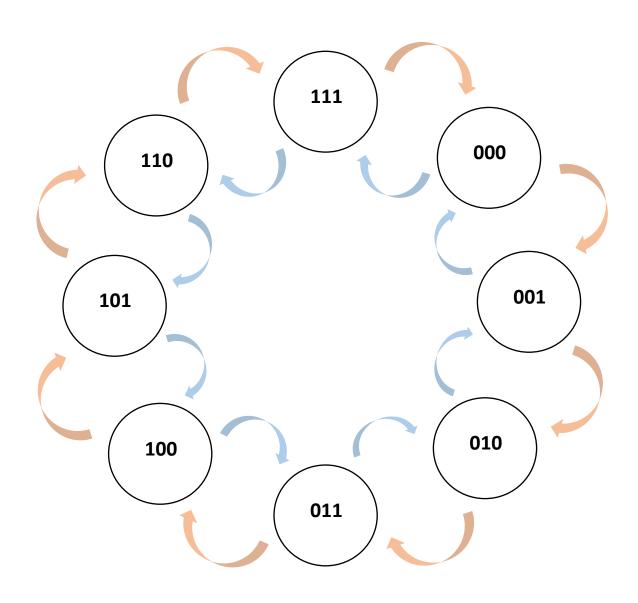


## **State table**

Present state	Next state	Flip- Flops input
A2 ,A1 ,A0	A2+ A1+ A0+	TA2, TA1, TA0
0 0 0	1 1 1	1 1 1
0 0 1	0 0 0	0 0 1
0 1 0	0 0 1	0 1 1
0 1 1	0 1 0	0 0 1
1 0 0	0 1 1	1 1 1
1 0 1	1 0 0	0 0 1
1 1 0	1 0 1	0 1 1
1 1 1	1 1 0	0 0 1

Present state	Next state	Flip- Flops input
A2 ,A1 ,A0	A2+ A1+ A0+	TA2, TA1, TA0
0 0 0	0 0 1	0 0 1
0 0 1	0 1 0	0 1 1
0 1 0	0 1 1	0 0 1
0 1 1	1 0 0	1 1 1
1 0 0	1 0 1	0 0 1
1 0 1	1 1 0	0 1 1
1 1 0	1 1 1	0 0 1
1 1 1	0 0 0	1 1 1

- Draw the k-maps and derive the logical expressions

## K map

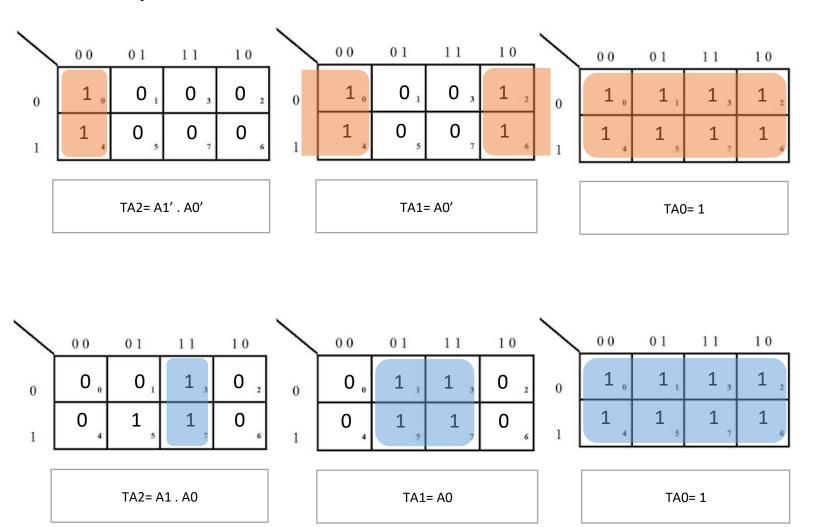

- Design and implement the circuit using Logisim.

Show your work below, include a picture of the final design from the simulator and submit the Logisim file as well.

